

Class 3

Ham Radio Technician Course

Leslie Rohde, N7LER • leslie@n7ler.com • Cell Phone:
512.207.0539



1

Electronics



2

Technician Level Electronics

- There are Sorta Two Kinds of Electricity
 - Direct Current (DC) and Alternating Current (AC)
- DC is Sorta Like Plumbing
- Ohm's Law
- DC Circuits and Schematics
- AC is Radio in Wires
- AC Circuits and Schematics



3

Electrical Plumbing

- A Battery is Like a Water Tower
- A Switch is Like an On-Off Valve
- A Resister is Like Pinching the Hose
 - Skinny Pipes Have More Resistance than Bigger Pipes
- A Potentiometer is Like a Gate Value (Variable Resistance)
- Increasing Resistance Decreases Flow (Current)
- Increasing Voltage Increases Flow (Current)



4

The Plumbing Analogy

- Voltage ~ Pressure (psi)
- Resistance ~ “Back Pressure” (psi)
- Current ~ Flow Rate (gpm)



5

Terminology

- Electromotive Force (EMF), abbreviated as “E”, is measured in Volts and is the Force that causes “electrons” to “flow”
- The resistance to that flow, and abbreviated by “R”, is measured in Ohms and written as the Greek letter Omega Ω
- The amount of “flow” is current measured in Amperes (Amps) and generally abbreviated as “I”



6

Just For Fun

- One ampere is the current in which one coulomb of charge travels across a given point in 1 second
- One coulomb is equal to about 6.241×10^{18} electric charges



7


Ohm's Law

$$E = I \times R$$



8

“The Magic Circle”

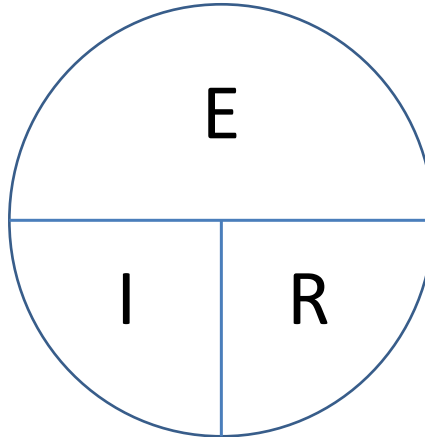

Using the “Magic Circle”

Ohm's Law & the Magic Circle

Your Granddaddy Ham likely knew that a chap named Georg Simon Ohm (1789-1854) experimented with electricity and discovered that the resistance of a conductor depends on its length in feet, cross-sectional area in circular mils, and its resistivity, which is a parameter that depends on the molecular structure of the conductor and its temperature. Sounds complicated, and it is, but his discovery allows us to calculate some important electrical measurements.

Ohm's Law ($E = I \times R$) states the relationship between voltage, current, and resistance in an electrical circuit. It says that the applied electromotive force (E) in volts, is equal to the circuit current (I) in amperes, times the circuit resistance (R) in ohms. The "magic circle" is an easy way to remember Ohm's Law and understand how to solve for E, I, or R when the other 2 quantities are known. Here is the magic circle and the 3 equations:

$E = I \times R$
Finding Voltage

$I = E \div R$
Finding Current

$R = E \div I$
Finding Resistance

To use the circle, cover the unknown quantity with your finger and solve the equation using the 2 known quantities. If you know the values of I and R and want to find the value of E, cover the E in the magic circle and it shows that you must multiply I times R. If you want to find I, cover the I and it shows that you must divide E by R. If you want to find R, cover the R and it shows you must divide E by I.

There is another "magic circle" to help you remember how to calculate power in a circuit. Power in watts (P) is equal to current (I) in amperes times volts (E) in volts. Use it the same way as the Ohm's Law magic circle; that is, cover the unknown quantity with your finger and perform the mathematical operation represented by the remaining quantities.


$P = I \times E$
Finding Power

$I = P \div E$
Finding Amperes

$E = P \div I$
Finding Voltage




A Simple Schematic

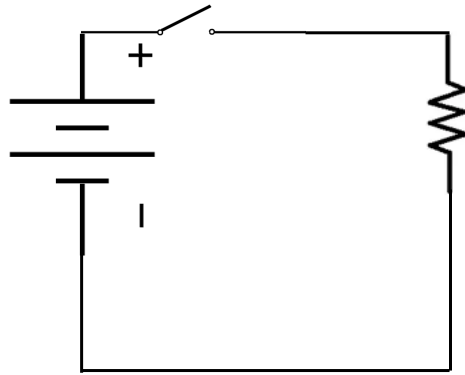


11

Applying Ohms Law

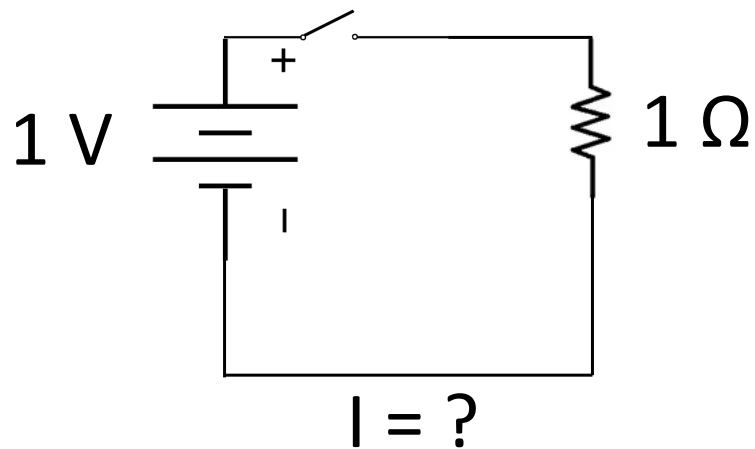


12

Applying Ohms Law

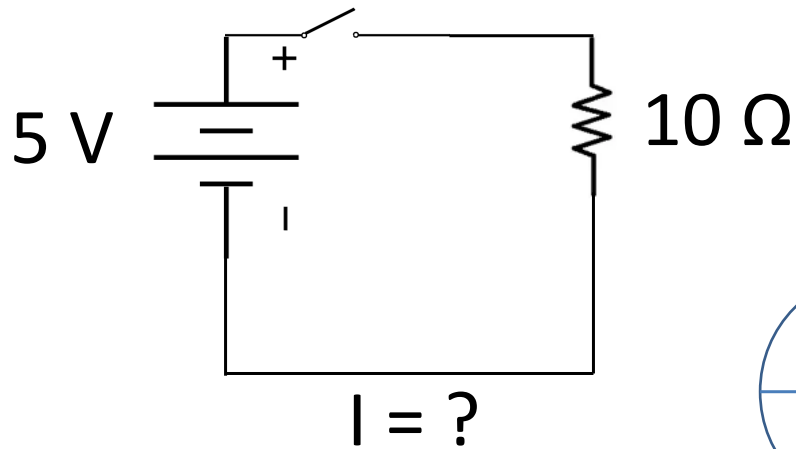


13

A Few Schematic Symbols

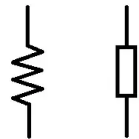

Resister

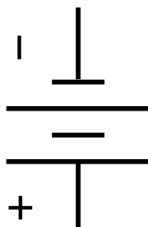


Battery



Switch



Diode

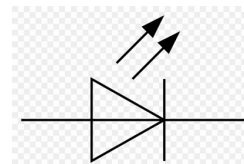


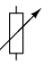

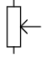







LED



14

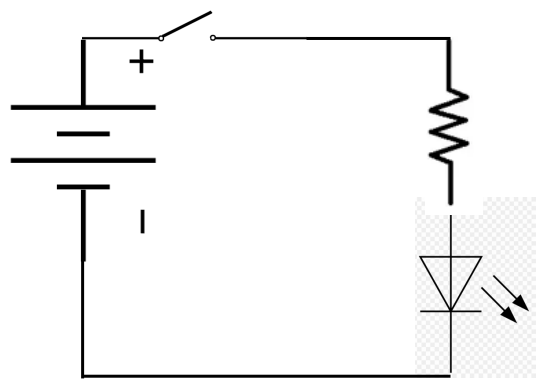

Resistors

Fixed-value	Rheostat
 	 
Potentiometer	Tapped Thermistor
 	 
Photoresistor	
	


15

A Flashlight

16

A Diode is a One-Way Valve

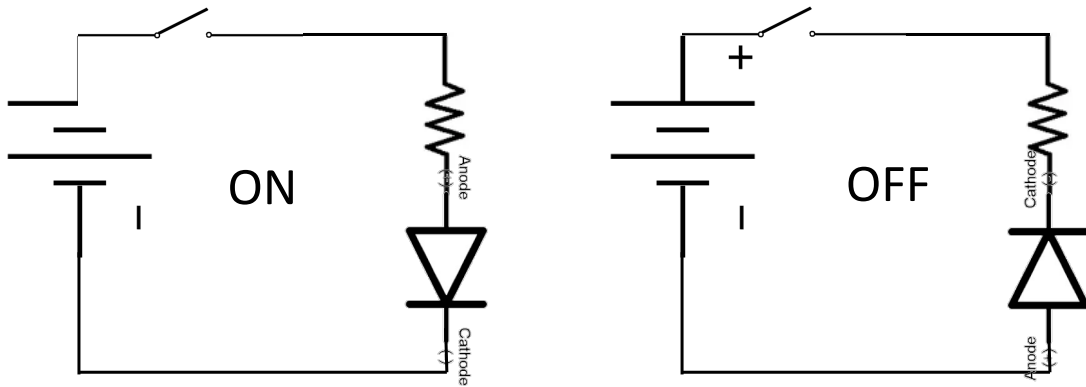

17

**Can you have a circuit
without a ground?**



18

Ground is Relative

- Chassis vs. Earth
- What is the very best ground?
- Is my ground your ground?
- Can you be a good ground?
- Wanna be?




19


Measuring Voltage and Current

Voltage is measured across the Source.

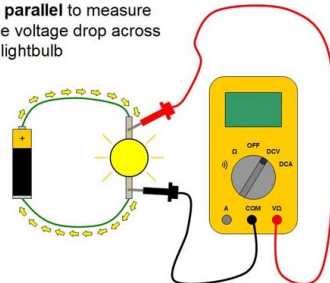Connect a multimeter in **parallel** to measure the voltage drop across a lightbulb



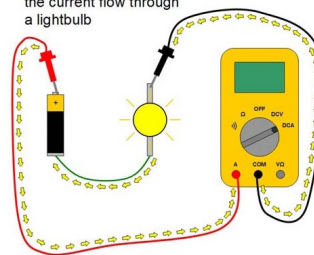Connect a multimeter in **series** to measure the current flow through a lightbulb




Current is measured with the meter in line with the source. “+” line to the positive and “-” to the “sink” side of the circuit.




20

Parallel and Series Circuits

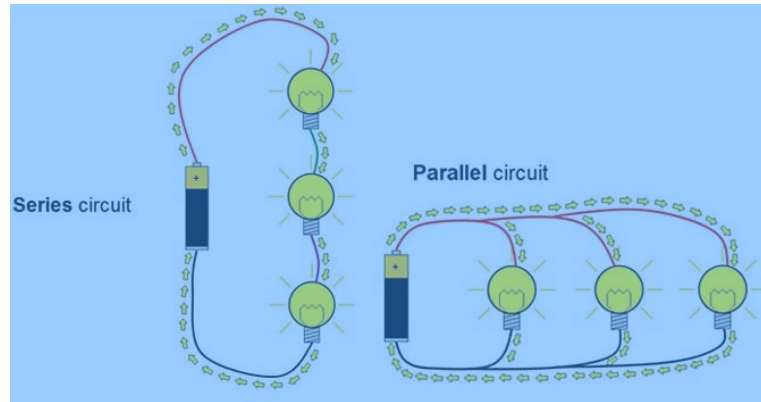


21

Series Resistors

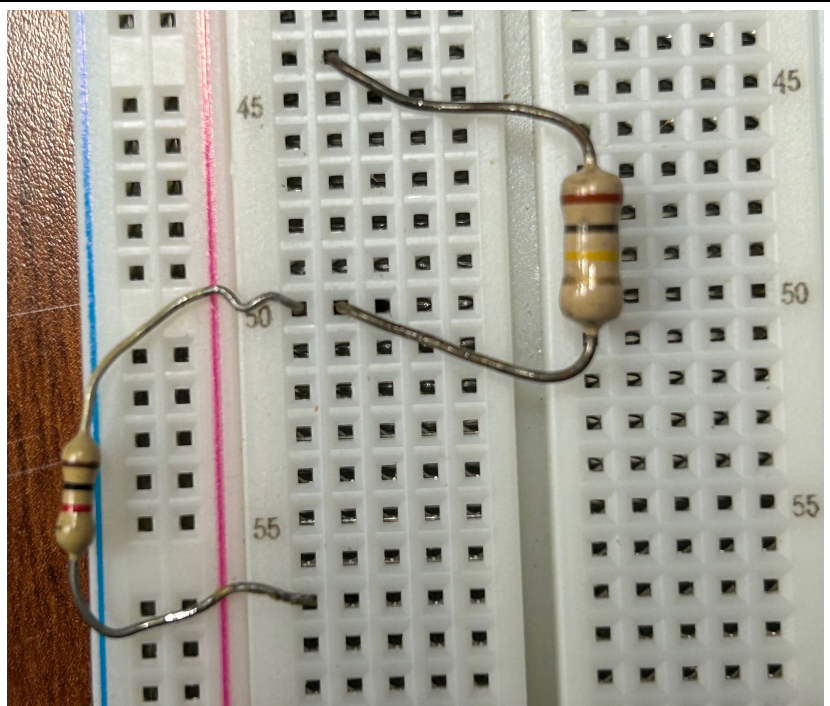

22

Parallel Resistors

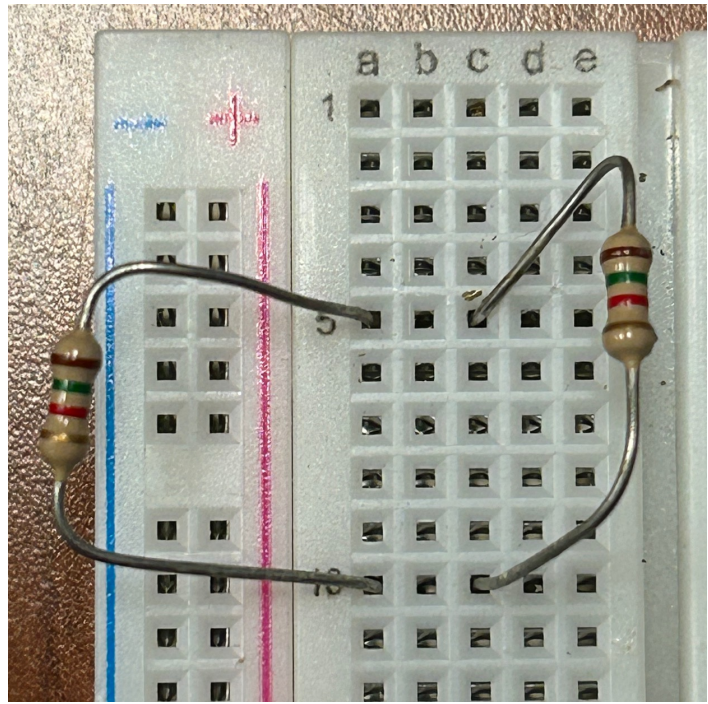

23

Power

- More Current (flow) can do more “work”
- More Voltage (pressure) can do more “work”
- Power is the product of voltage and current
- The unit of power is the Watt
- One Watt = 1 Volt times 1 Amp



24

High Pressure x Low Current



25

Low Pressure x High Current




26

High Pressure x High Current




27

The Other “Magic Circle”

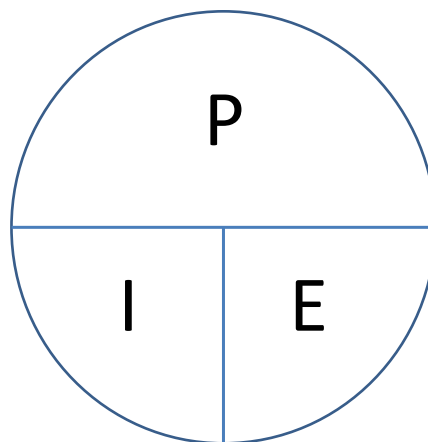

28

How Much Power is Dissipated?

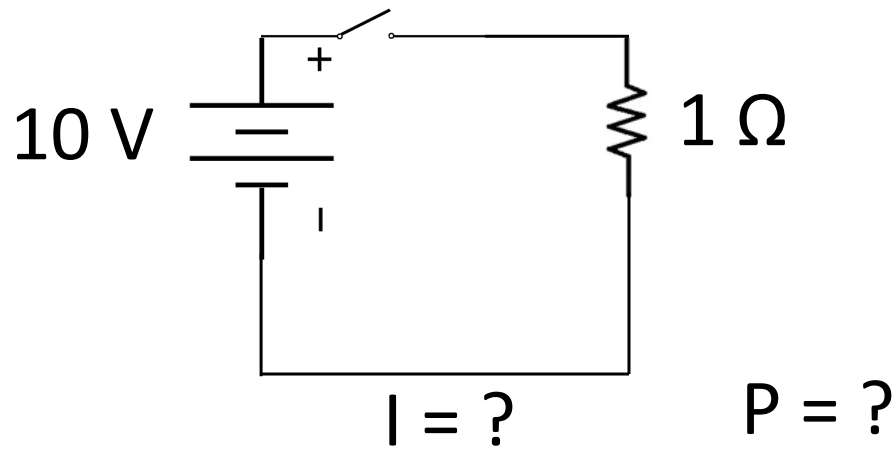



29

Semiconductors




30

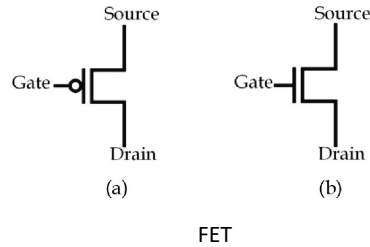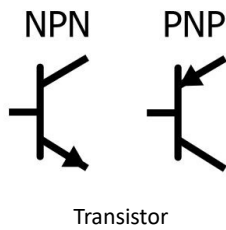Transistors are Electrically Variable Resistors




31

Simple Transistor Circuit

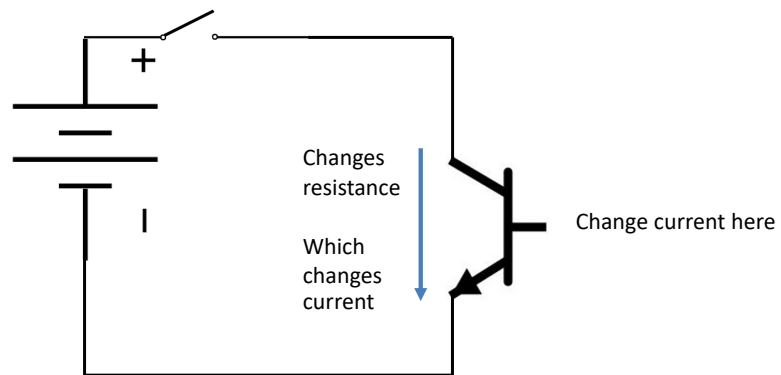


32

NPN and PNP Transistors

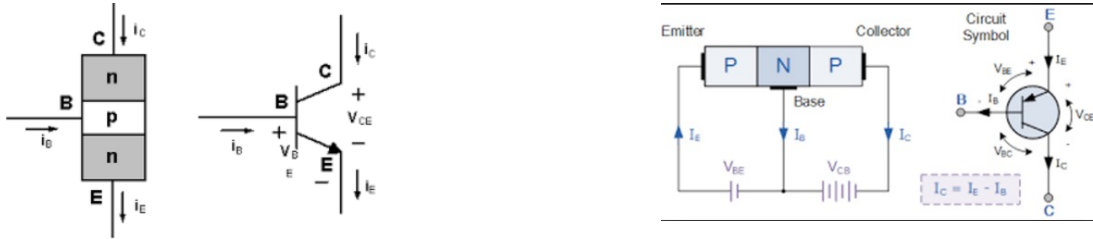


NPN = **N**ever **P**oints **i**n

Positive Voltage

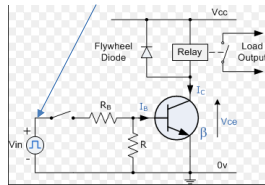

Schematic Symbol is usually written with the base on the left, but the Collector and Emitter can be either up or down

Negative Voltage

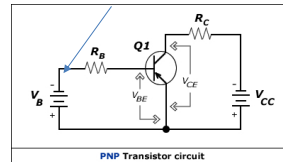

AC Electronics



The “Plumbing” Metaphore No Longer Works Very Well




35

Ohm’s Law Still Applies at Each Instant in Time




36

Suppose We Had a Variable Battery

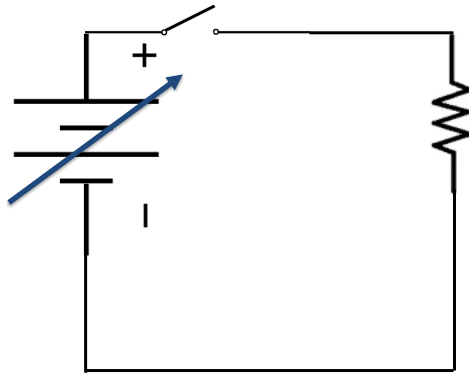


37

Suppose We Had a Variable Battery

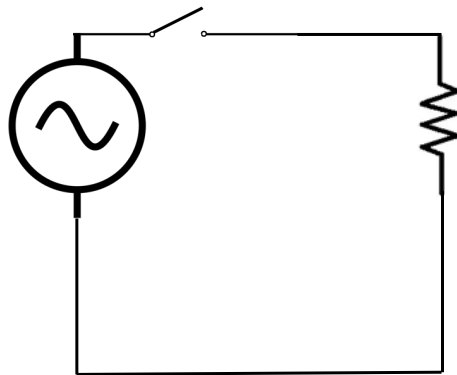


38

As Voltage Changes, So Does Current

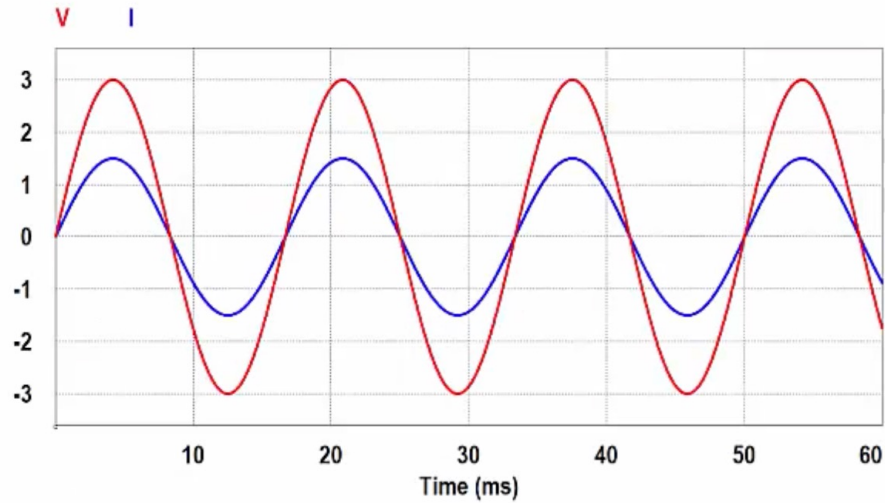

39

Electro-Magnetic Waves

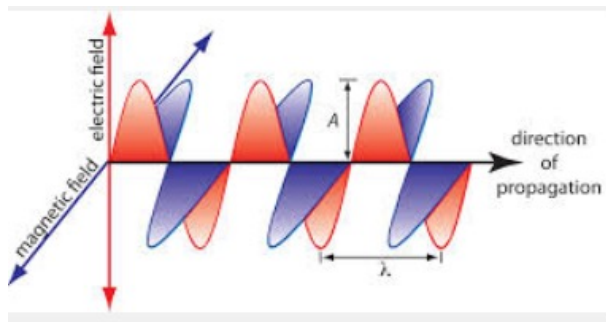

Wave length = distance peak to peak
 All radio has both electrical and magnetic fields



40

Can You Have Just an Electric Wave?




41

Can You Have Just a Magnetic Wave?



42

AC is Radio in Wires

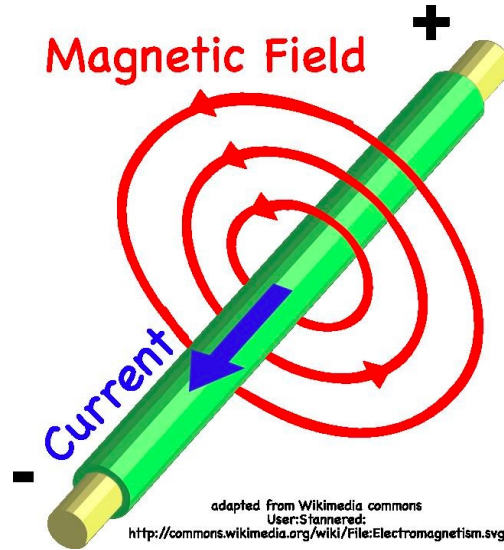


43

All Wires Leak AC



44

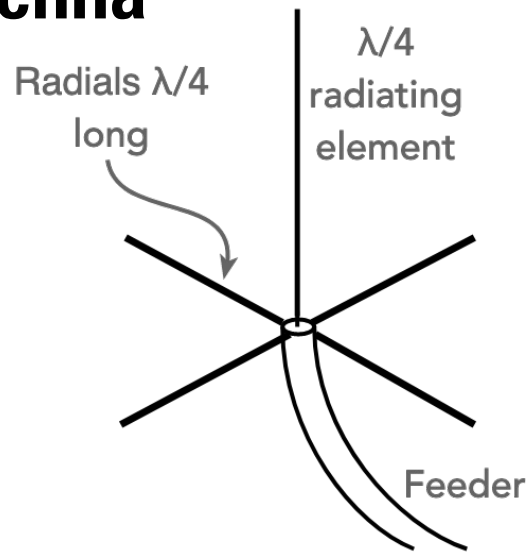An Intentionally "Leaky" Wire We Call an Antenna



45

Capacitors Store Energy
as Electric Charge




46

Change the Area of Overlap to Change the Capacity




47


AC Components

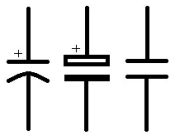


Capacitor

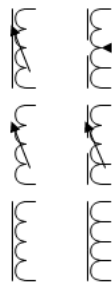

Coils

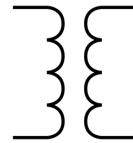

Transformer

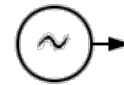


Oscillator




Crystal



48

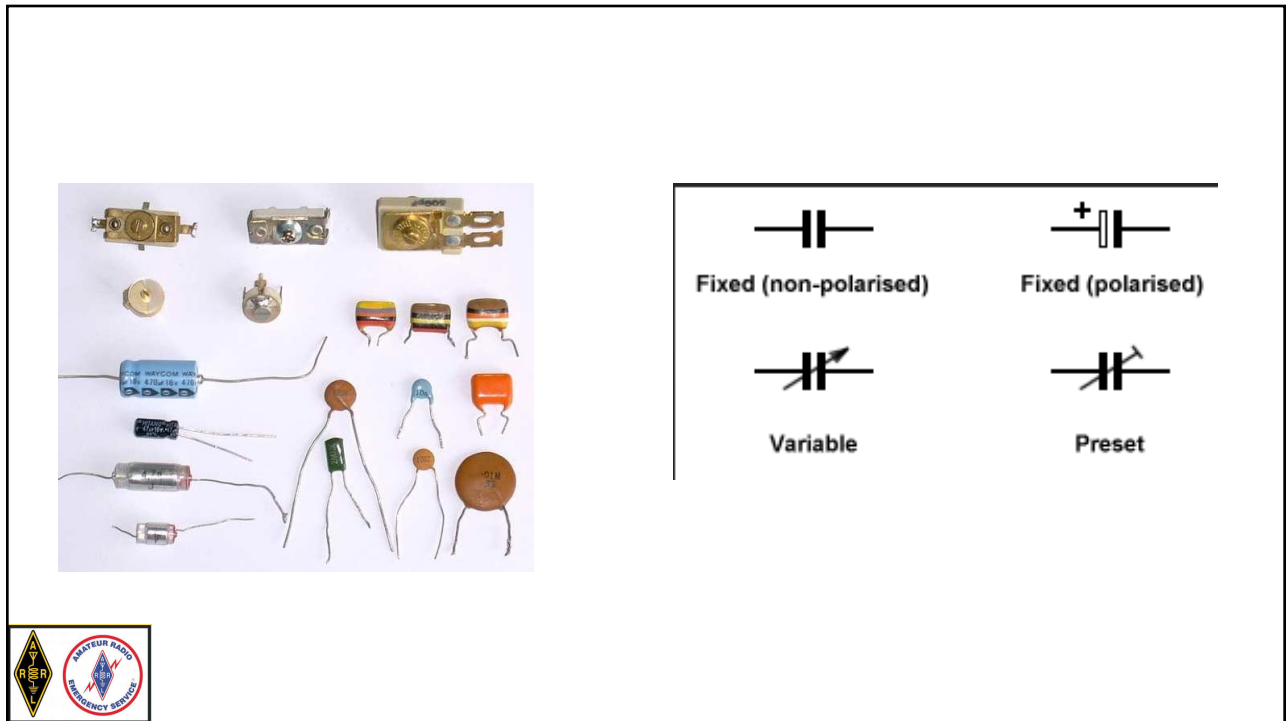


49

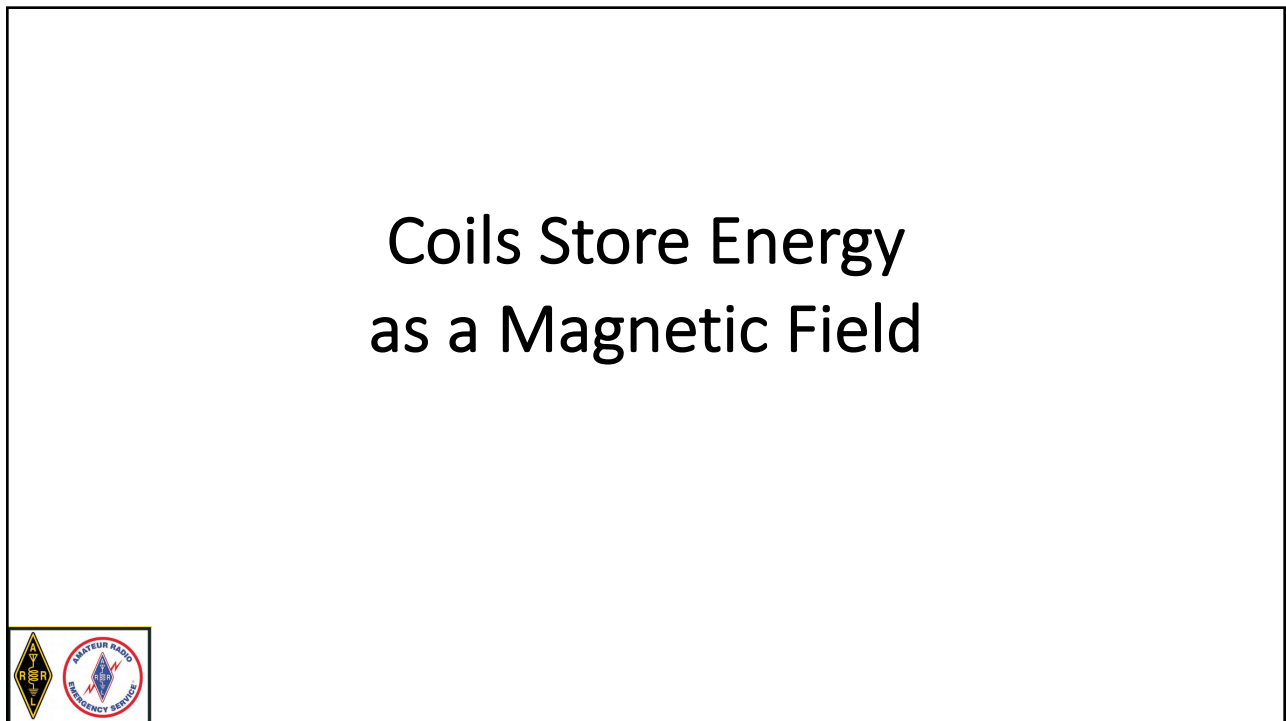


50

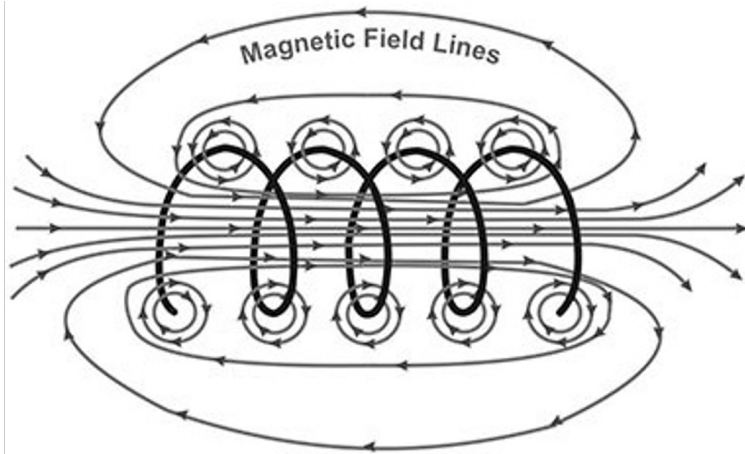More Overlapping Fields Creates Greater “Resistance to Change” (Reactance)



51

Coils (

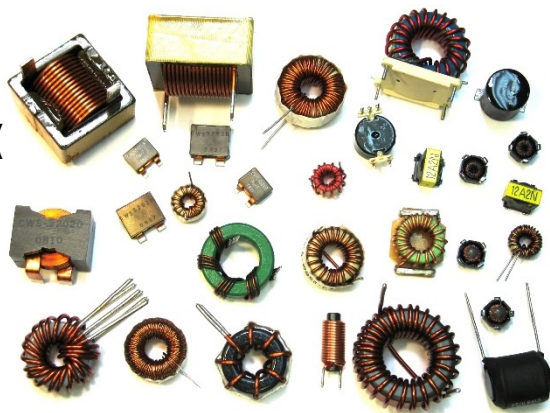


52

Transformers



53

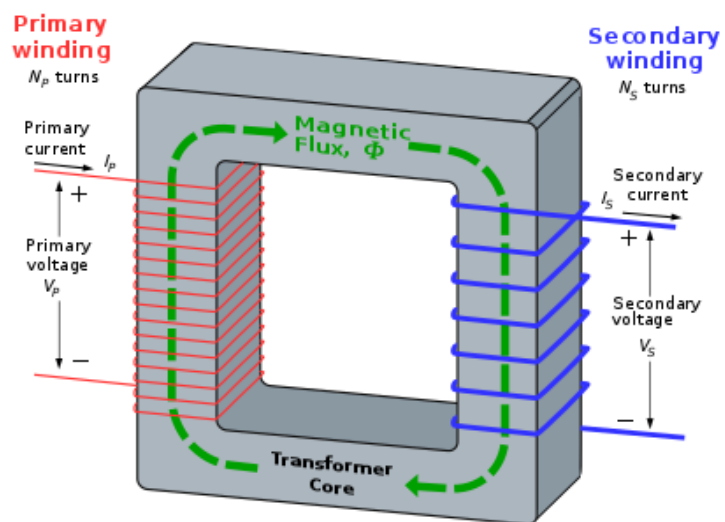Transformers are Coils Talking to Each Other



54

Electrical Schematics and symbols

Electrical Schematic Symbols

Most used symbols in Radio


- Resistors
- Capacitors
- Diode
- Transistors
- Coils
- Switches
- Relays
- Plugs
- Ground
- Antennas
- Connections

Most of these come in fixed value or variable.

Combining capacitors and inductors (coils) makes a tuned circuit.




One Transistor Radio

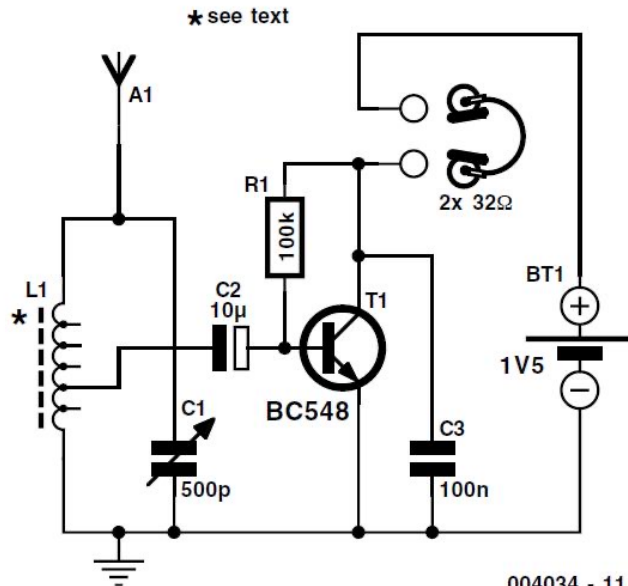

004034 - 11



A Simple FM Transmitter

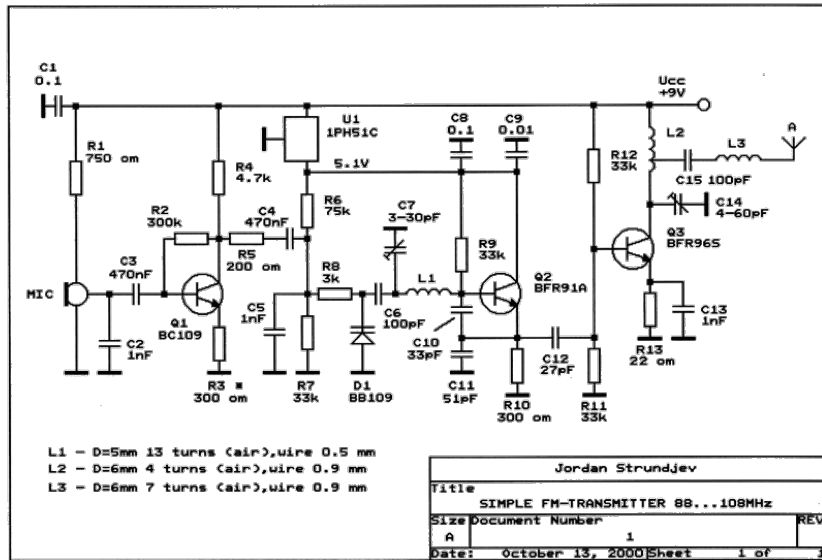

Antennas Our Most Special Electrical Component



Resistance Resists DC



59


Reactance/Impedance Resists AC



60

Inductors

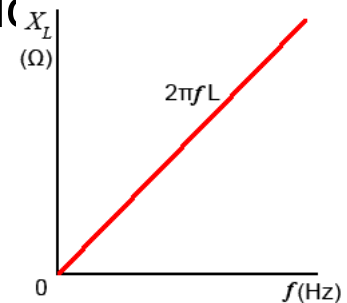
- Zero resistance to DC
- Increasing reactance with frequency
- Also called inductance or inductive reactance



61

Capacitors

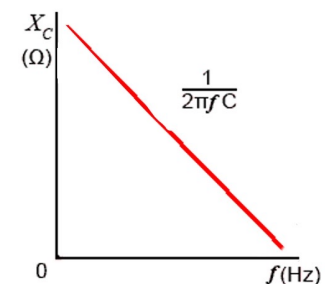- Infinite resistance to DC
- Decreasing reactance with frequency
- Also called capacitance or capacitive reactance



62


Tuned Circuits

- Combine inductance and capacitance
- Circuit will resonate at (theoretically) one frequency
- A crystal resonates because it is both inductive and capacitive
- At Resonance, Capacitance = Inductance



63

Tuned Circuits

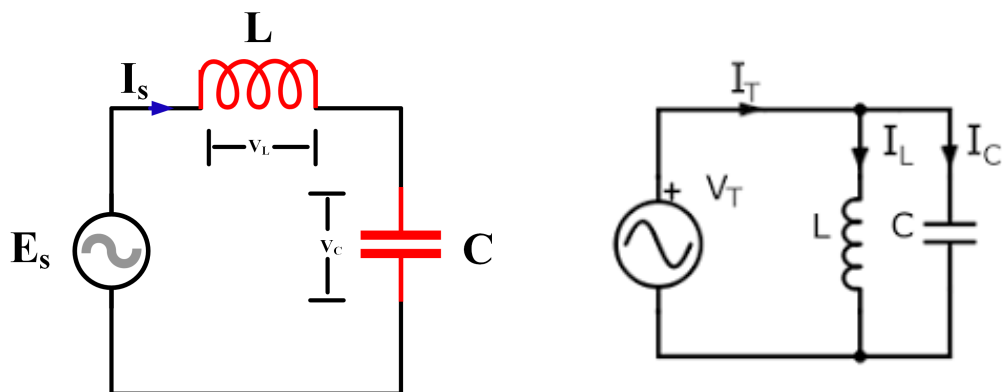

64

Everything has Impedance



65

**Even "Empty Space" has Impedance
(about 377 ohms)**



66

Everything in the Universe Will Resonate at Some Frequency

HINT: RF Safety



67

Revisiting EM Waves

- EM waves permeate all space
- EM waves permeate all matter
- EM = RF = AC
- AC currents in wires radiate EM into space
- EM waves in space induce AC currents in wires



68

Antennas

- All wires are "leaky"
- Antennas are optimized for leakiness at a selected frequency
- Best transmit frequency = best reception frequency
- This is the "resonance" frequency
- Antennas are Tuned Circuits



69

Even EM Waves Have a Ground



70


Guided Wave = AC in Wire

Unguided Wave = EM Radiation



71


Electro-Magnetic Waves

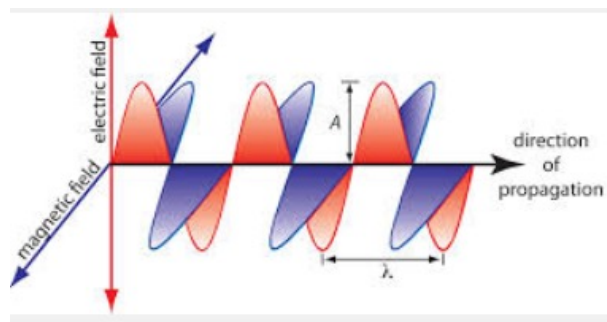


Wave length = distance peak to peak
All radio has both electrical and magnetic fields



72

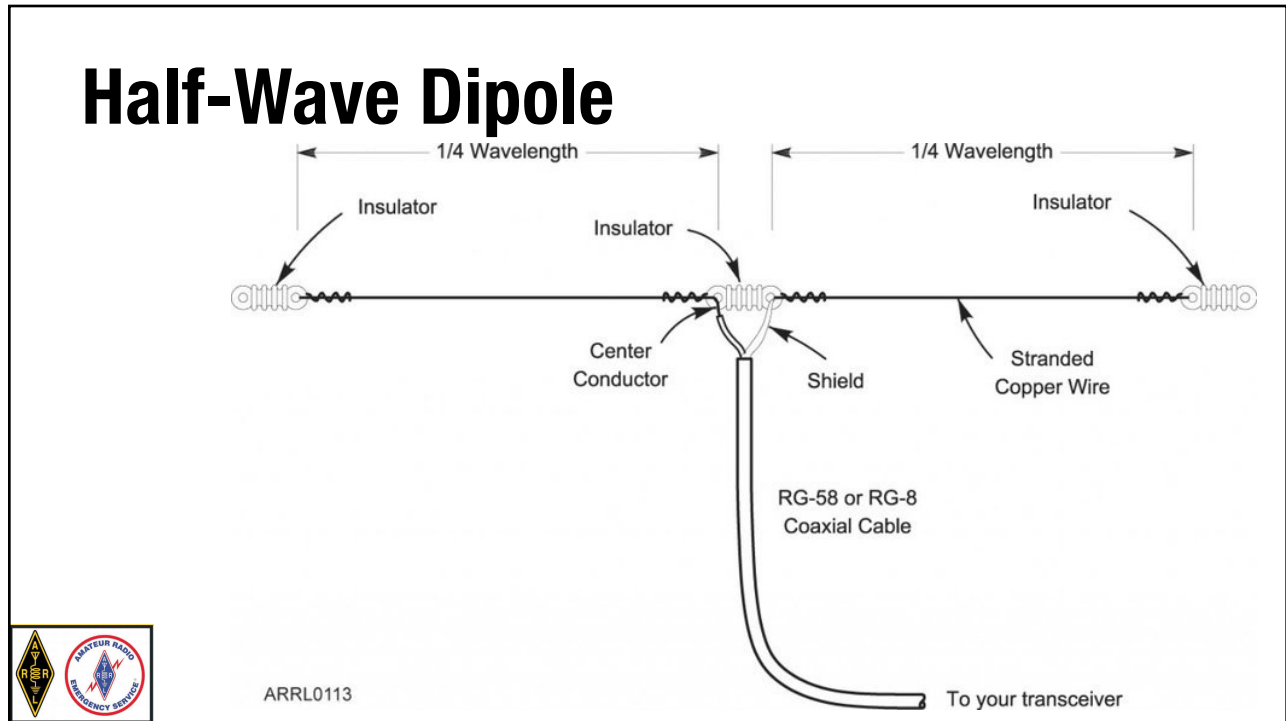


73

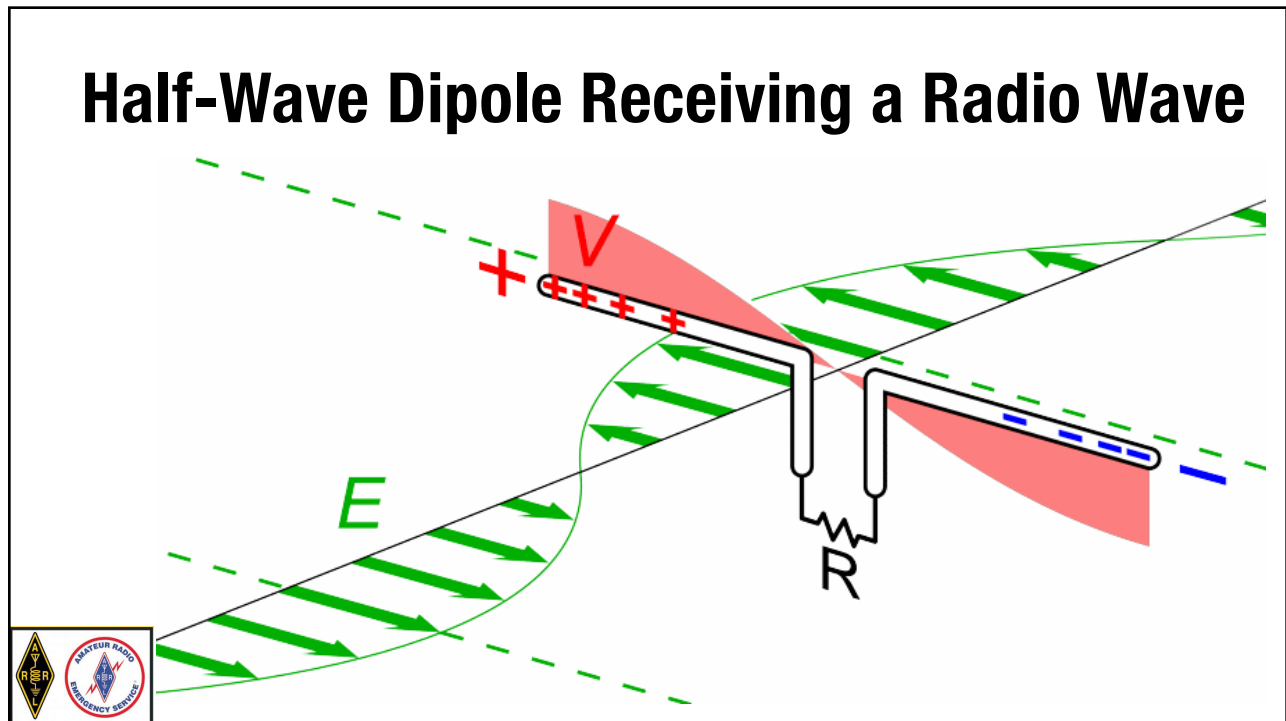

74

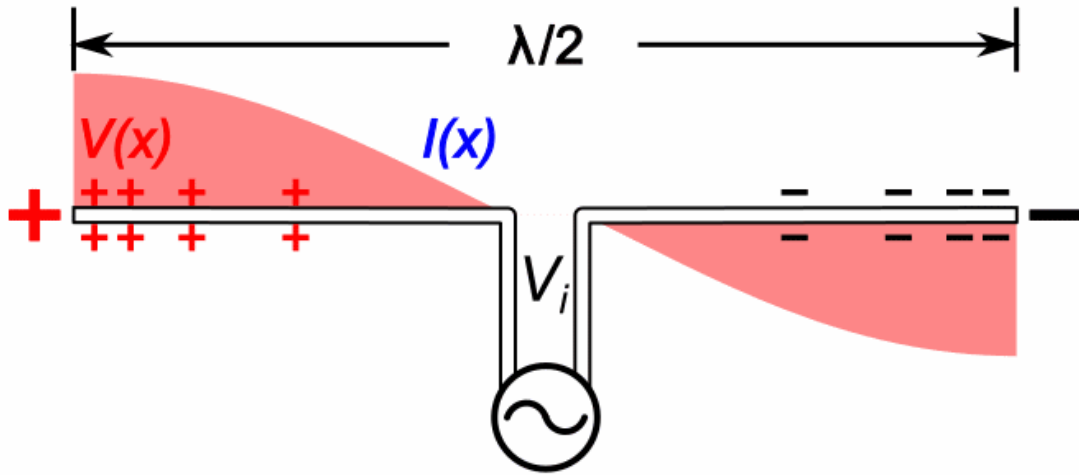Voltage vs. Current in a Transmitting Antenna





75

EM Wave Polarization


The orientation of the Electric field

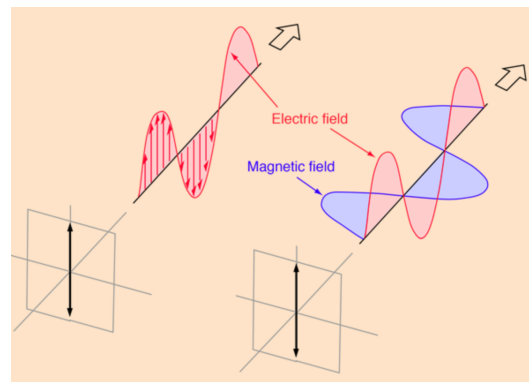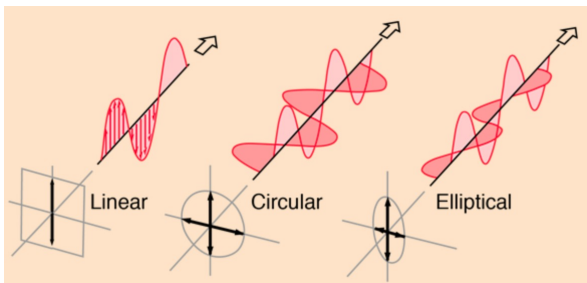- Horizontal
- Vertical
- Circular? Elliptical??



76

Half-Wave HORIZONTAL Dipole

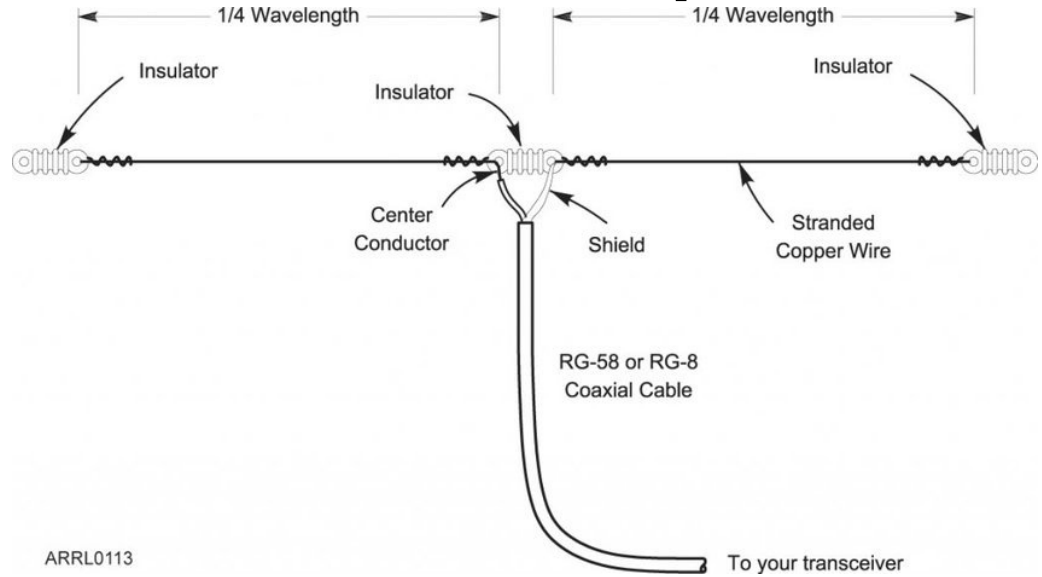


77

Antenna Radiation Patterns



78

Horizontal Dipole Radiation Pattern

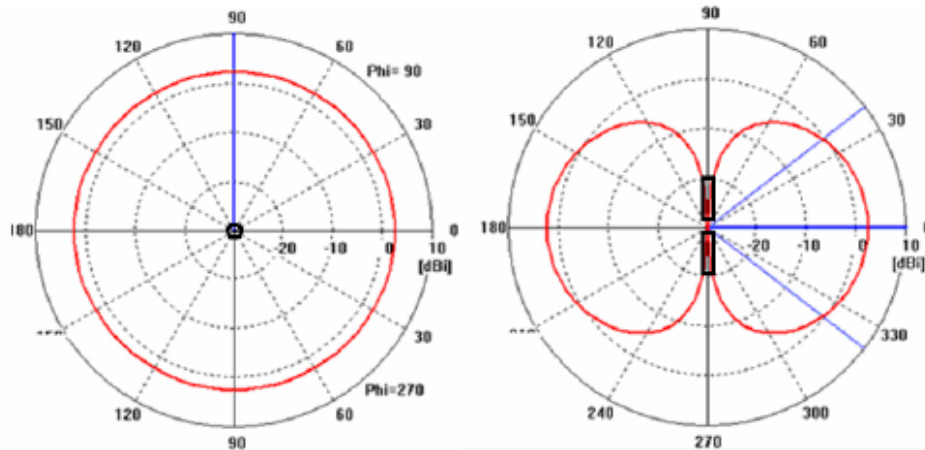

Side, End-On View

Top View



79

Vertical Monopole Antenna

- Where's the other half of the antenna?
- You need a ground plane
- Like the roof of a car
- Any car?




80



81

Antenna Gain

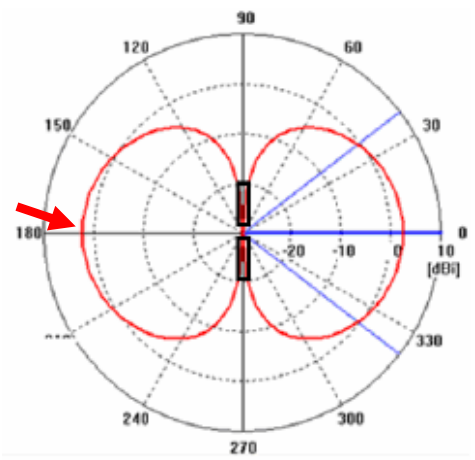- All Gain is Relative (dbi)
- Directional Antennas are "Concentrators"
- Even the Dipole has a tiny amount of gain




82

Yagi



83

Yagi

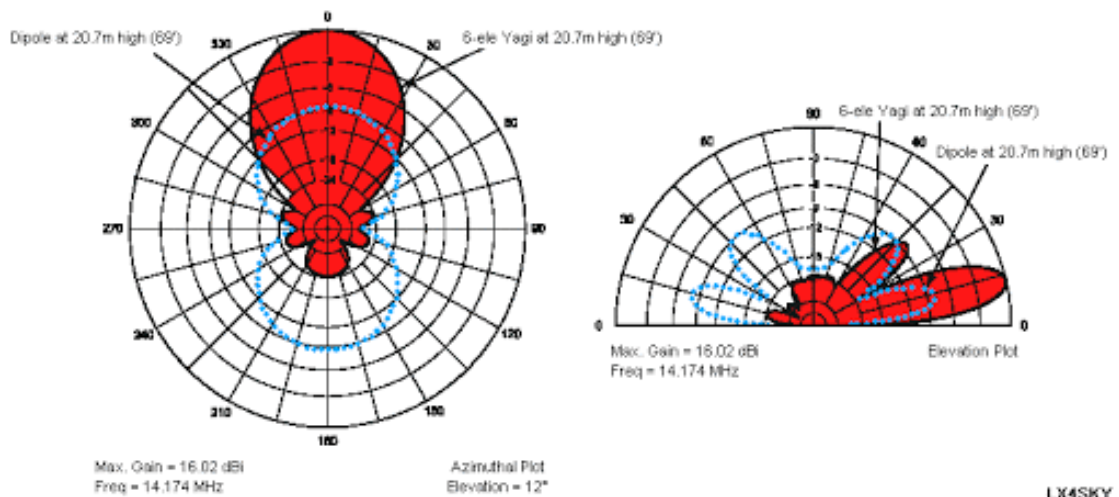

84

How the Yagi Works

The diagram illustrates the operation of a Yagi antenna. On the left, a circular wave pattern shows 'in phase constructive interference' in the forward direction and 'out of phase destructive interference' in the backward direction. The antenna elements are labeled D1, D2, E, and R. On the right, a schematic shows the 'Driven element' and 'Director'. Below, four waveforms represent: 'Driven element emission' (green), 'Director emission' (blue), 'Backward emission' (light blue), and 'Forward emission' (dark blue). The forward emission waveform is significantly larger than the others, indicating the antenna's directional gain.

85

Slim Jim

UHF 440-470 MHz Slim Jim Antenna
 ★★★★★ (4 customer reviews)
 \$37.00 - \$41.00

Are you looking for a UHF omni antenna with a little more gain? Our UHF Slim Jim Antenna delivers up to 6dbi of gain on the 440 - 470 Mhz UHF bands, which is almost twice the gain of a J-Pole and 5 times the gain of a 1/4 wave ground-plane antenna. Plus the antenna also have the great low noise floor and wide bandwidth typical of our other antennas.

UHF Slim Jim Antenna 440-470MHz 440-450MHz Amateur Radio


connector SO-239 Clear

\$37.00

1 Add to cart

www.jpole-antenna.com

86

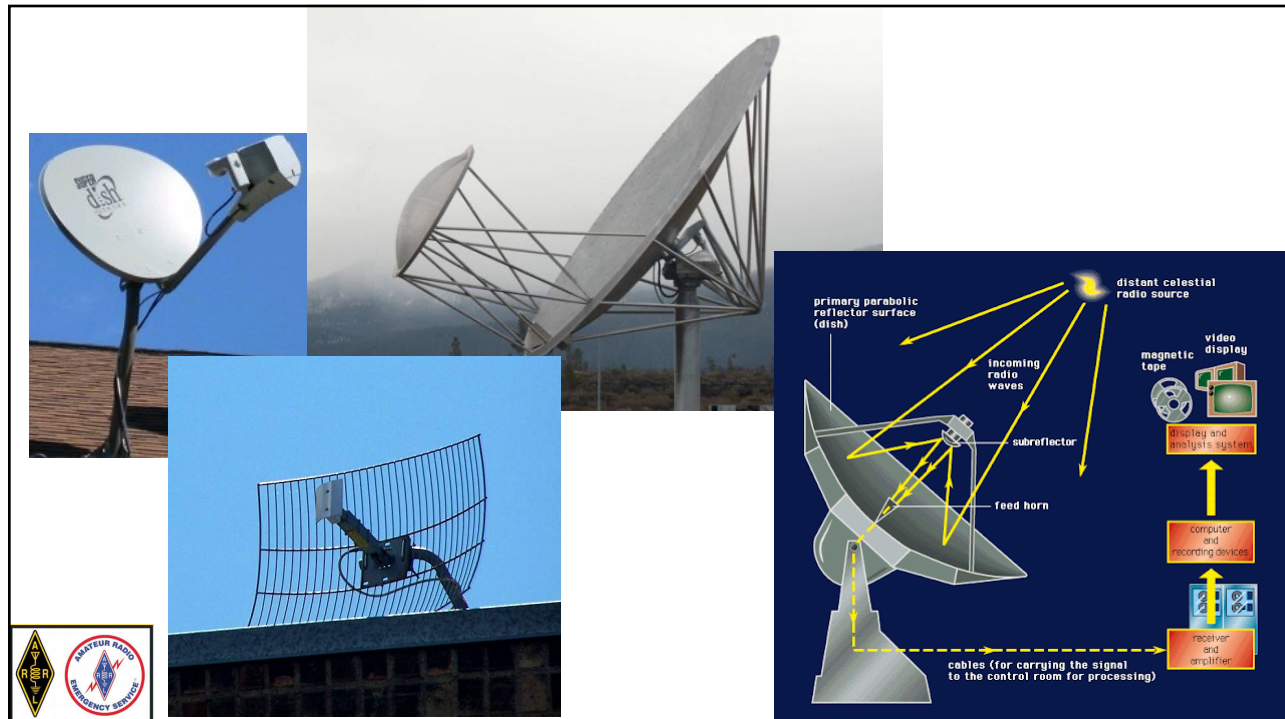

87

Just a Few Types of Antennas

- Half-wave Dipole
- Quarter-wave vertical
- 5/8-wave vertical
- Yagi
- Dish
- Hourglass loop



88

Logarithmic Units



89

WHY?



90

Use a Calculator

- $\text{dB} = 10 * \log_{10}(\text{power ratio})$
- Power ratio = 2:1
- $\text{Log}_{10}(2) = 0.3$ 3db
- $\text{Log}_{10}(10) = 1$ 10db



91

Or Just Know These Common Values

- 3db = 2x
- 6db = 4x
- 9db = 8x
- 10db = 10x



92

dB of What?

- dBi – compared to a (theoretical) “isotropic antenna”
- dBm – compared to 1 mW
- dBv – compared to 1 mV



93


Test Yourself

- Prior to 2003, spurious emissions had to be 40 dBm or lower
- Post 2003, this was changed to 43 dBm

- How much difference is that in linear units?



94

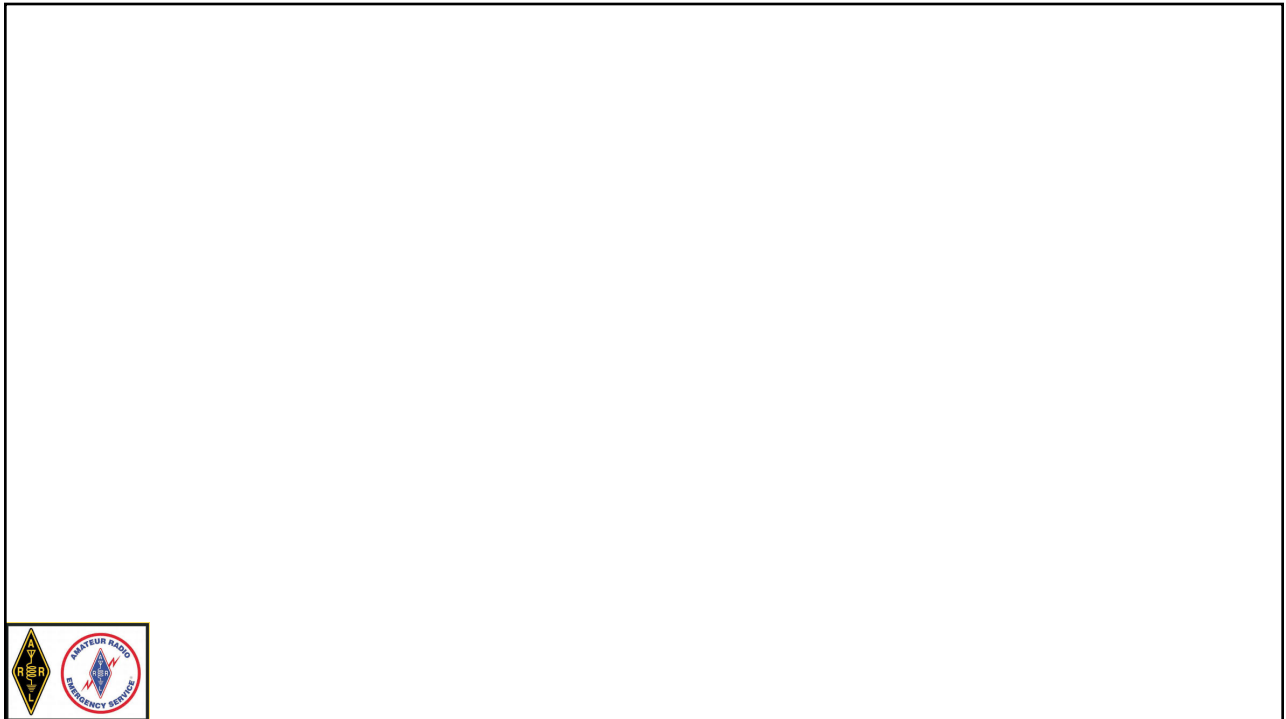

95



Moving Up to General




96

Parallel vs. Series Components




97


In Series

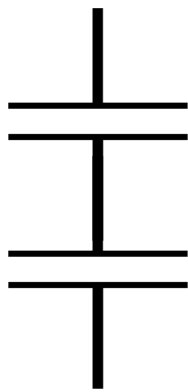

Special

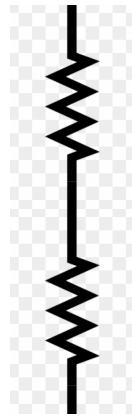

Just Bigger

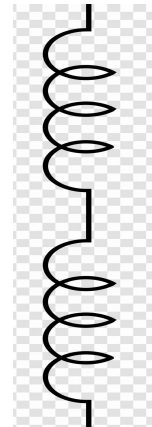


Just Bigger




98


In Parallel

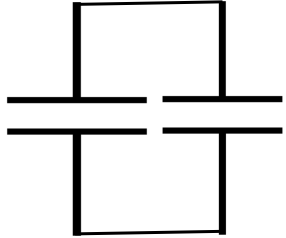

Just Bigger

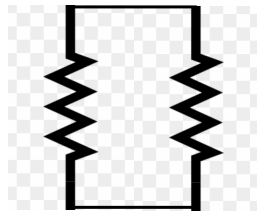

Special

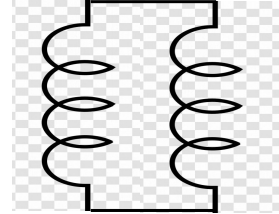

Special



99

The “Special” Ones

$$X_{\text{total}} = \frac{1}{\frac{1}{X_1} + \frac{1}{X_2} + \frac{1}{X_3} + \dots}$$



100

Computing Parallel Resistance

$$R_{\text{total}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$



101


Computing Parallel Coils

$$L_{\text{total}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$



102

Kirchhoff's Laws

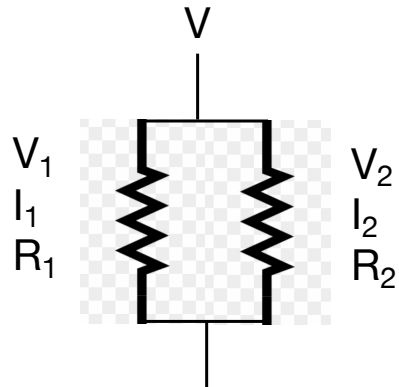

Force applies equally: $V = V_1 = V_2$

Charge/Current is conserved: $I = I_1 + I_2$



103

RMS Voltage

- Stands for “Root Mean Squared”
- the “amount of AC power that produces the same heating effect as an equivalent DC power”
- $V_{\text{RMS}} = 0.7071 * V_{\text{peak}}$
- $0.7071 \sim 1/\sqrt{2} = (\sqrt{2})/2$



104

Gravitational Potential Energy

$$\text{PE grav.} = m \times h \times g$$

Where:

- **PE grav.** - Gravitational potential energy of an object;
- **m** - Mass of the object in question;
- **h** - Height of the object; and
- **g** - Gravitational field strength acting upon the object (1 g or 9.81 m/s² on Earth).



105

Electric Field ~ Gravity Field

- When a battery is connected into a circuit, the excess of positive and negative charges at the battery terminals cause an electric field to exist in the circuit.
- Electrons in the circuit have electric potential energy because of their position in the electric field; there is a difference in electric potential energy (a 'potential difference' or a 'voltage') between any two points in the circuit.
- Charge gains electric potential energy as it passes through the battery; this is transformed into other energy forms as charge moves around the circuit.
- 'Voltage' is about differences in electric potential energy for each charge. This is very helpfully reinforced by using 'joule per coulomb' instead of 'volt' when measuring voltage.
- The greater the voltage, the greater the electric field in a circuit and the greater the electric potential energy per charge transformed as charges move in the circuit.



106

Electrical Potential Energy

Electric Potential Difference

The **electric potential difference** between points **A** and **B**, $V_B - V_A$ is defined to be the change in potential energy of a charge **q** moved from **A** to **B**, divided by the charge. Units of potential difference are joules per coulomb, given the name volt (V) after Alessandro Volta.

$$1 \text{ V} = 1 \text{ J/C} \quad (7.3.2)$$



107

Definitions

Volt:

1 Joule of energy per Coulomb of charge

Ampere:

1 coulomb of charge moving past a point
in one second



108

Power = Energy/Time

- $1 \text{ Watt} = (1 \text{ Joule/Coulomb}) * (1 \text{ Coulomb} / 1 \text{ s})$
- $V = 1 \text{ Joule/Coulomb}$
- $A = 1 \text{ Coulomb} / 1 \text{ s}$

- $1 \text{ Watt} = \text{Volt} * \text{Amp}$

