

Class 5

Ham Radio General Supplement

Leslie Rohde, N7LER • leslie@n7ler.com • Cell Phone:
512.207.0539



1

Almost Done!

- Review
- Rectifiers
- Modulation, Deviation, and Bandwidth
- Transformer turns ratio [optional]



2

Rectifier


- Changes AC to DC
- Three Types
 - Half Wave
 - Full Wave
 - Full Wave Bridge



3


Half Wave Rectifier

Half Wave Rectifier

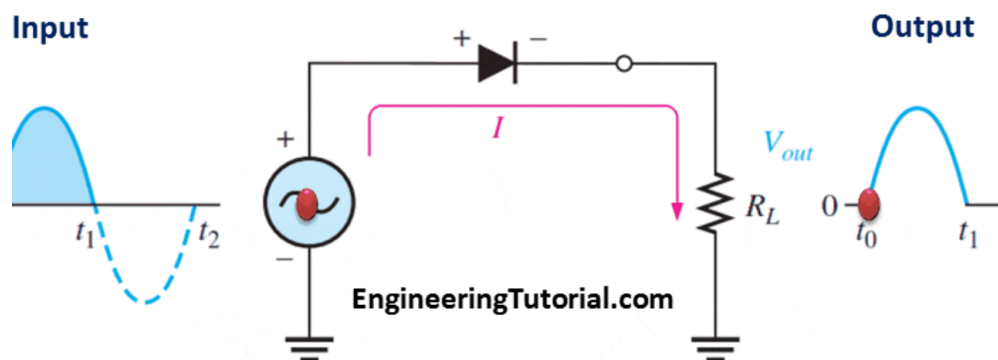

4

Full Wave Rectifier


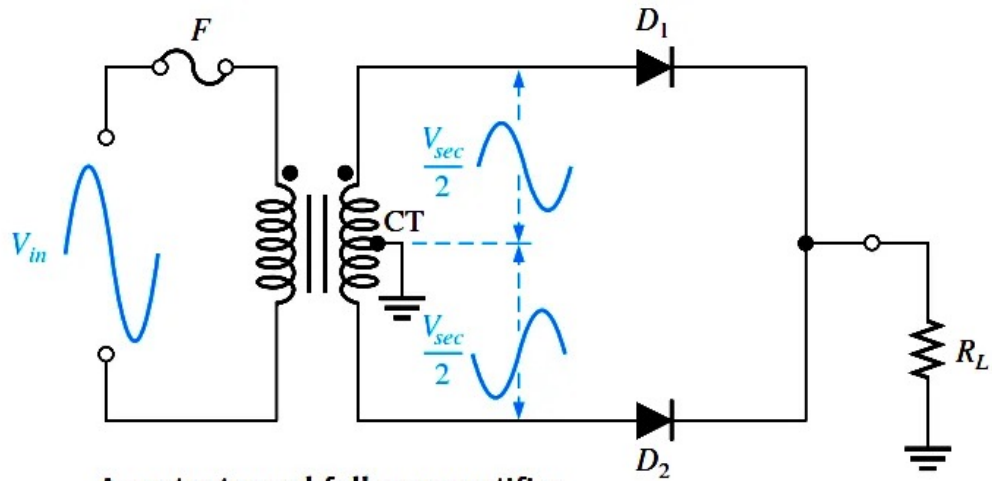


A center-tapped full-wave rectifier




5

Full Wave Rectifier

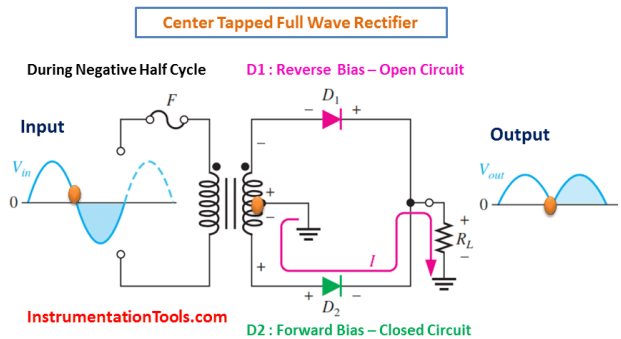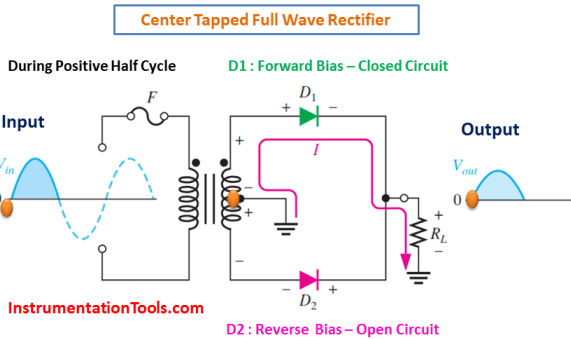

6

Bridge Rectifier

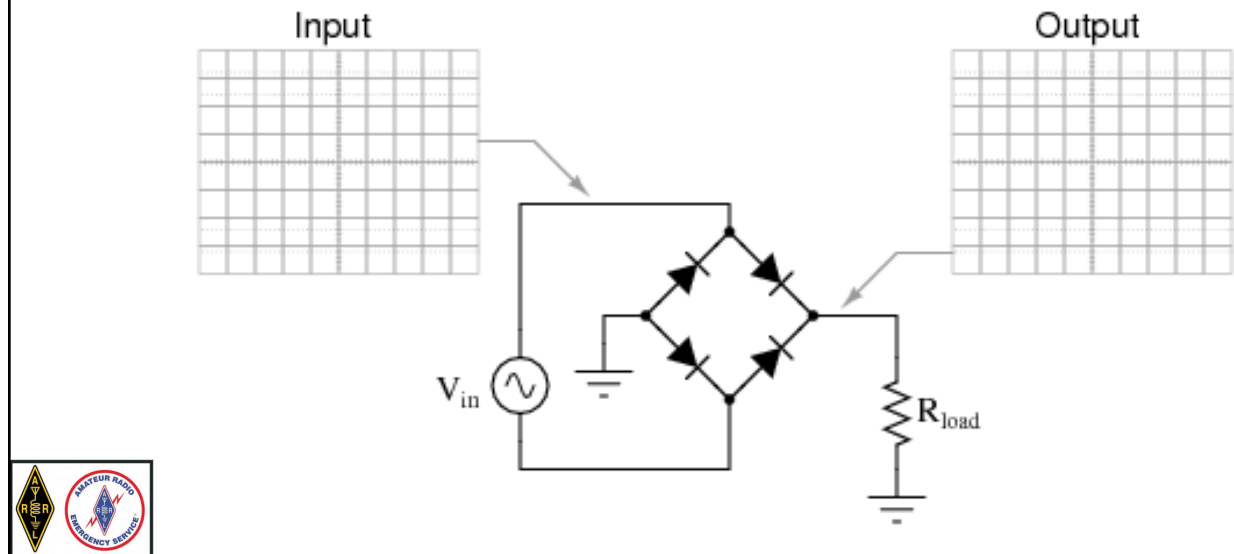

7

FM Audio Modulation

- Audio frequency deviates the carrier
- The amplitude also deviates the carrier
- They add!



8

Carson's Rule

Peak deviation [a transmitter design parameter]

Plus

highest modulation frequency [enforced by filters]

All multiplied by two



9

Question G8B06

“What is the total bandwidth of an FM-phone transmission having a 5kHz deviation and a 3kHz modulating frequency?”

$$(5 + 3) \times 2 = 16\text{kHz}$$



10

Question G8B02

“What is the total bandwidth of an FM-phone transmission having a 5kHz deviation and a 3kHz modulating frequency?”

$$(5 + 3) \times 2 = 16\text{kHz}$$



11

Question G8B07

“What is the frequency deviation for a 12.21 MHz reactance modulated oscillator in a 5 kHz deviation, 146.52 MHz FM phone transmitter?”

Divide deviation by ratio of frequencies


$$146.52/12.21 = 12$$

$$5/12 = 0.4167\text{kHz} = 416.7 \text{ Hz}$$



12

Reactance Modulator

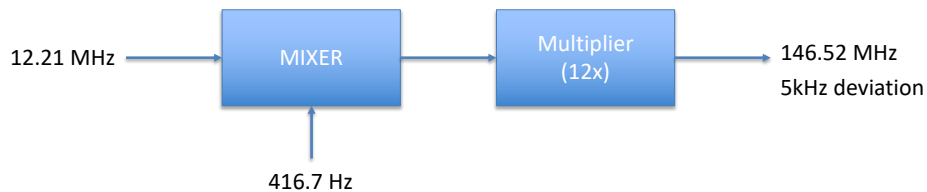

$$146.52\text{MHz}/12.21\text{MHz} = 12$$

$$5\text{kHz}/12 = 0.4167\text{kHz} = 416.7 \text{ Hz}$$



13

Question G8B02

“If a receiver mixes a 13.800 MHz VFO with a 14.255 MHz received signal to produce a 455 kHz intermediate frequency (IF) signal, what type of interference will a 13.345 MHz signal produce in the receiver?”

Image Response



The IF is the difference of the signal and VFO

14

Question G5C07

“What is the turns ratio of a transformer used to match an audio amplifier having 600 ohm output impedance to a speaker having 4 ohm impedance?”

$$\sqrt{600/4} = 12.1$$



100% derivable with just Ohms law!